



UNITED STATES
AIR FORCE
ACADEMY

ECE 383 - Embedded Computer Systems II Lecture 12 - Datapath and Control



Lesson Outline

- ~~Three Keys~~
- HW# 8 Due
 - CpE's and device drivers or HW interface
 - Ready, Scan, CW, SW?
- GR Lesson ~~14~~ 17
 - Example code and Mini-C
- ~~2-Line Handshake~~ Skip this year
- Datapath and Control – BRAM
- Lab 2 Next Lesson!
 - Show schematic
- ~~Packages~~ [not required anymore]

CHECK GRADES IN BLACKBOARD


HW 8b2?



| | | | | |
|-----|--|------------------------------|------------------------|--------------------|
| L9 | Finite State Machines | 10.2.1, 10.3.2, 10.4, 10.6.1 | Lab1 Write-up HW #6 | COB L9 BOC L10 |
| L10 | Datapath and Control | 11.1, 11.2, 14.4.2 | HW #7 | BOC L11 |
| L11 | Datapath and Control | 11.5 | HW #8 | BOC L12 |
| L12 | Datapath and Control | | HW #8b2 | BOC L13 |
| L13 | Lab2 - Data acquisition, storage and display | | Gate Check 1 | COB L13 |
| L14 | Lab2 - Data acquisition, storage and display | | Gate Check 2 | COB L14 |
| L15 | Lab2 - Extra lesson added this year | | Gate Check 3 | COB L15 |
| L16 | Lab2 - Data acquisition, storage and display | | Lab2 Functionality | COB L16 |
| L17 | GR #1 | | | |
| L18 | Soft CPU | | Lab2 Write-up HW #9 | COB L18 BOC L19 |



Mini-C to DataPath and Control

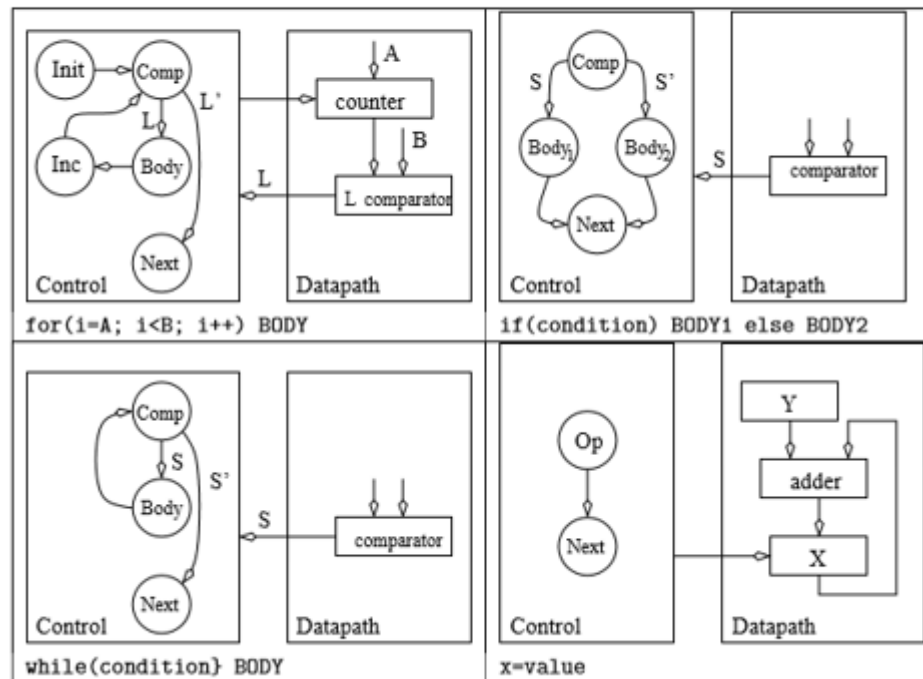




Given on GR

Example

BBBs

Combinational




Results are instantaneous (almost)

 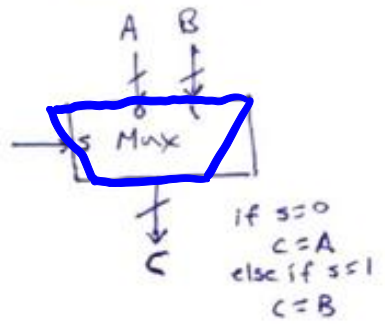 

Sequential (Register-based)

for simplicity, can assume all resets hooked to Global Reset and all clocks hooked to Global clock

Results appear on rising clockedge.

   

HW8: Ready, Scan, CW, SW?

- Datapath and Control Design Methodology
 - Datapath - responsible for data manipulations
 - Control - responsible for sequencing the actions of the datapath

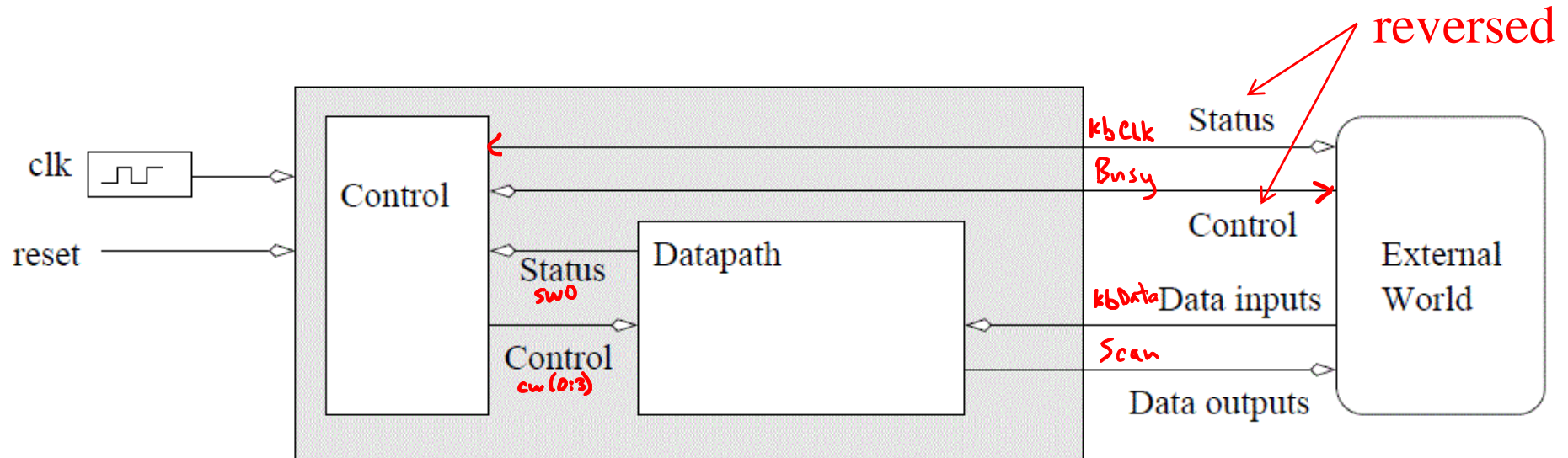


Fig 10.0 - An abstract digital system constructed from a datapath and a control unit.





- **Bring your calculator. No sympathy if you don't.**
- **Clock and Reset on diagram?**
- **Two states or one state?**
- **Decoding clock, low and high**
 - **Can you make a 4-state FSM to track the rise and fall of a clock?**

for syncing with and decoding a received clock signal



FSM

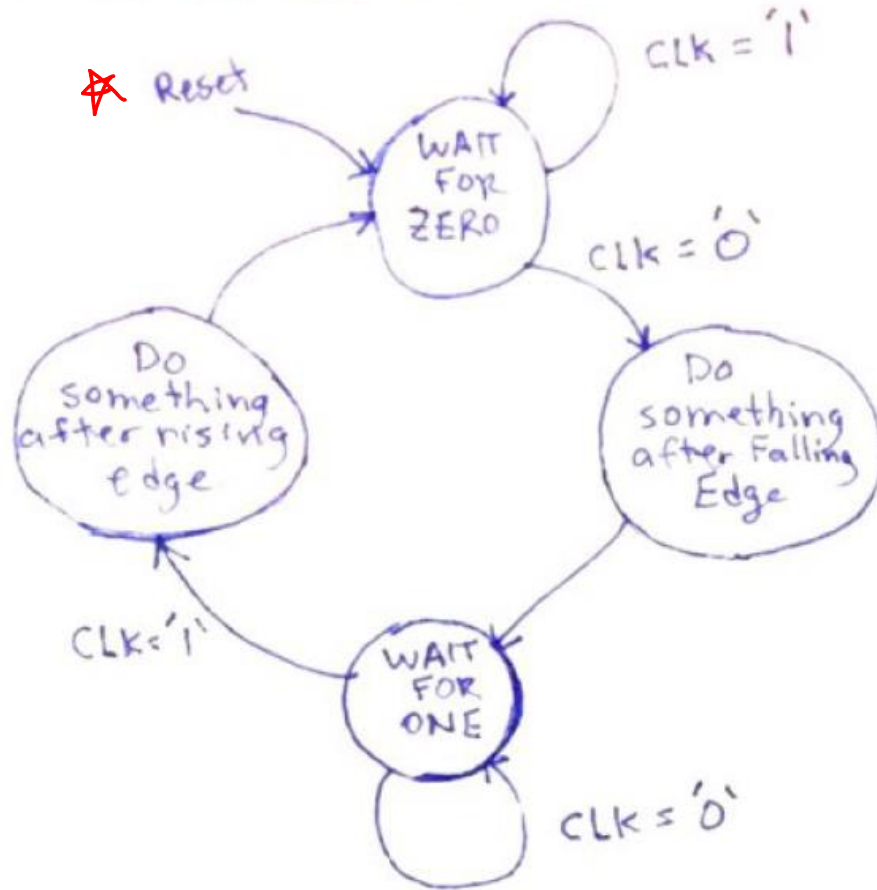
 
for syncing with and decoding a received clock signal



GR: two states or one state?

If you are designing a FSM controlling a datapath, and you need to do some action (from the controller) and then store the result, this takes two states (not one state).

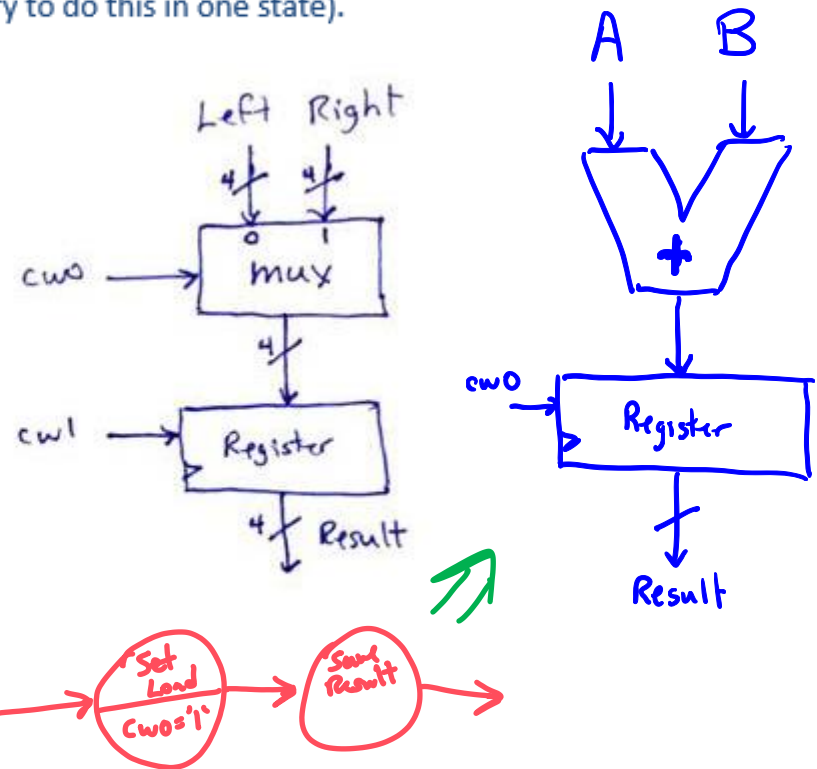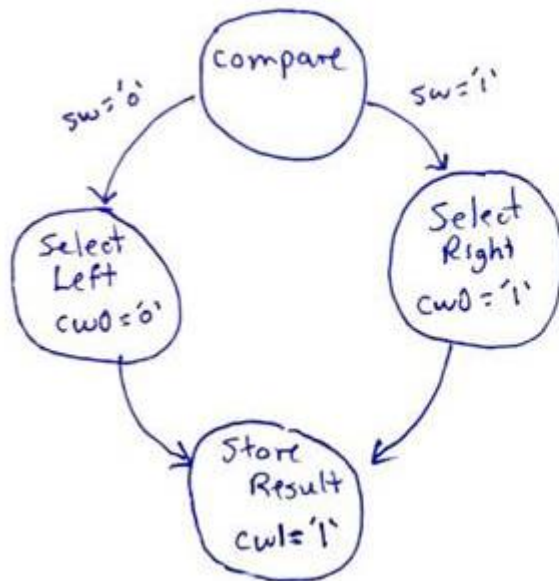For example, see the diagram below. The action is selecting "left" or "right", and then storing the value in the variable called "result". Takes two states! (I've seen students try to do this in one state).



Sometimes an action and storing can take just one state, when the action does not require a signal from the controller (because combinational logic is just real-time computing the action). For example, suppose the action is an ALU computation (real-time combinational logic), and the result of the ALU computation just needs to be stored in a register. This required just one state → load register.


(Whoops! This assumes cw0 already is '1' [Load], from previous state!)



UNITED STATES
AIR FORCE
ACADEMY

Datapath and Control - BRAM

LAB 2

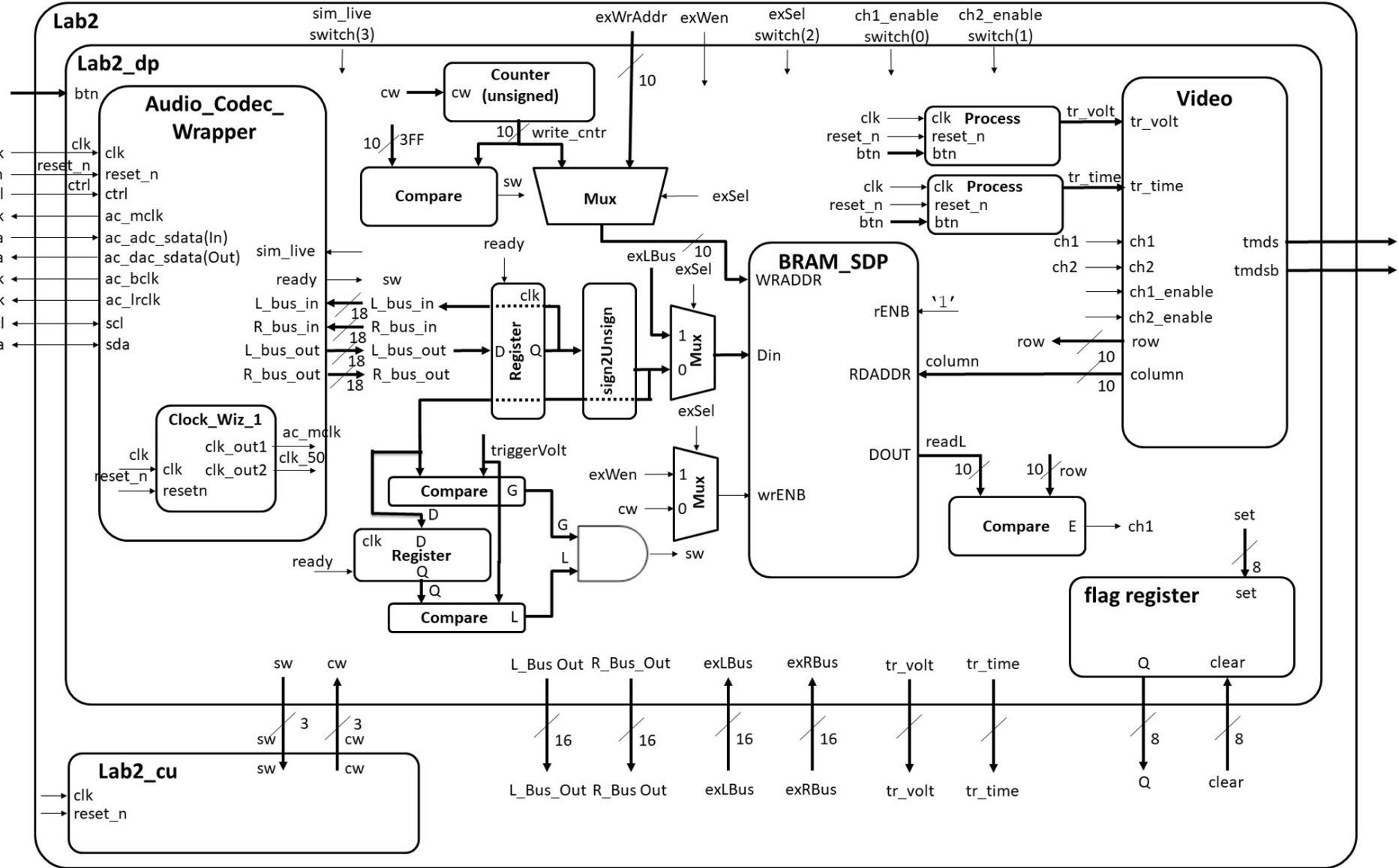

Datapath and Control - BRAM

- Artix 7 FPGA
 - First page of 7 Series Family Overview:
https://www.xilinx.com/support/documentation/data_sheets/ds180_7Series_Overview.pdf
 - Third page lists quantities how many of these resources our Nexys Video boards have.
 - For reference we are using the XC7A200T chip and the SBG484 package.

Datapath and Control - BRAM

- In our upcoming Lab2, you will need a large RAM to store 18-bit audio samples streaming in from the ATLYS board.
- The Xilinx FPGA on our board, a Artix 7, contains built in block RAMs (BRAMs).
- You can select of the three main BRAMs configuration (BRAM_SDP_MACRO, BRAM_SINGLE_MACRO, BRAM_TDP_MACRO) available in the UNIMACRO library.
- We will be using a BRAM_SDP_MACRO in our design.
- According to [Vivado Design Suite 7 Series FPGA Libraries Guide](#):


Datapath and Control - BRAM

- FPGA devices contain several block RAM memories that can be configured as general-purpose 18Kb or 36Kb RAM/ROM memories.
- These block RAM memories offer fast and flexible storage of large amounts of on-chip data.
- Both read and write operations are fully synchronous to the supplied clock(s) of the component.
- However, READ and WRITE ports can operate fully independently and asynchronously to each other, accessing the same memory array.
- Byte-enable write operations are possible, and an optional output register can be used to reduce the clock-to-out times of the RAM.

Datapath and Control - BRAM

Macro: Simple Dual Port RAM

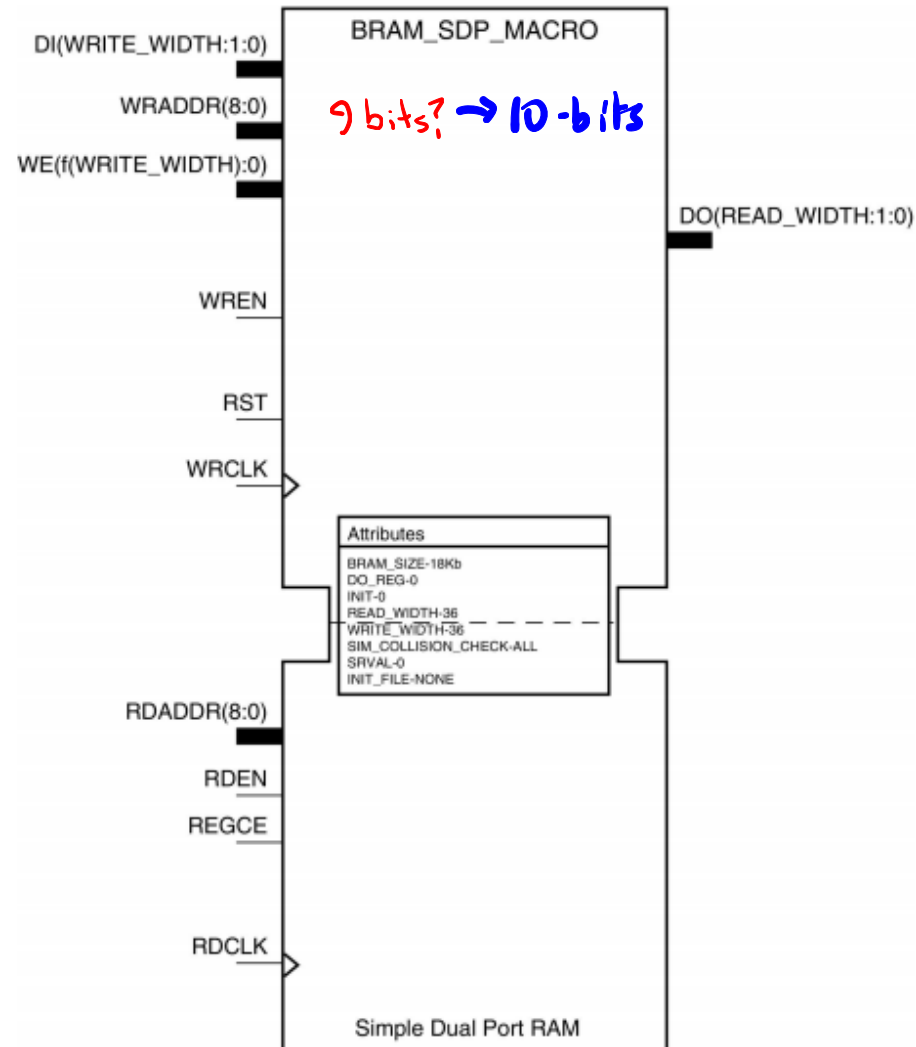- This is a schematic symbol of BRAM memory.
- Notes:
 - Inputs are on left
 - Outputs are on the right.
 - Left top side - write functions
 - Left bottom - the read functions
- The three types of BRAMs are highly configurable, but may be overwhelming to the new designer.




BRAM read/write


Read


state 1

state 2

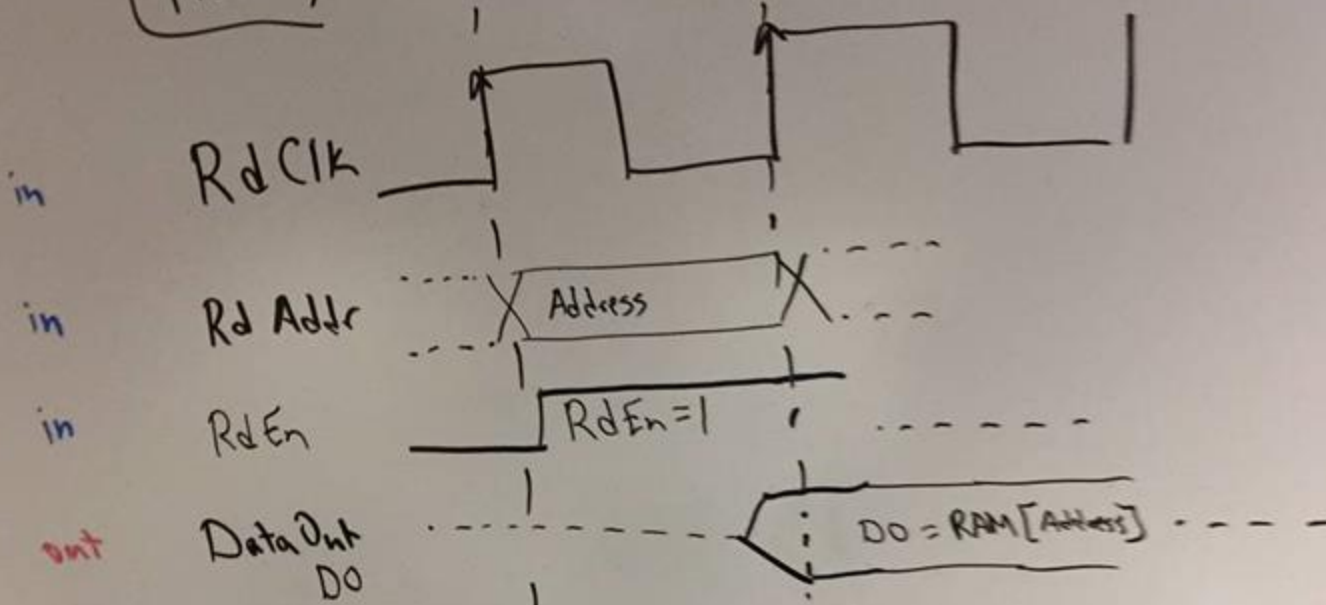

WRITE

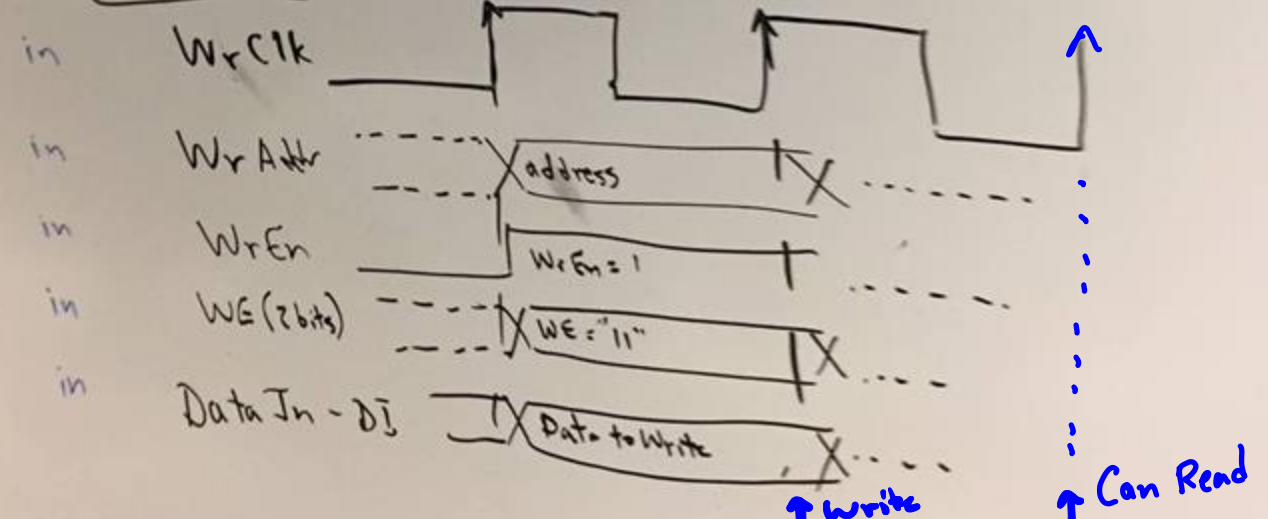

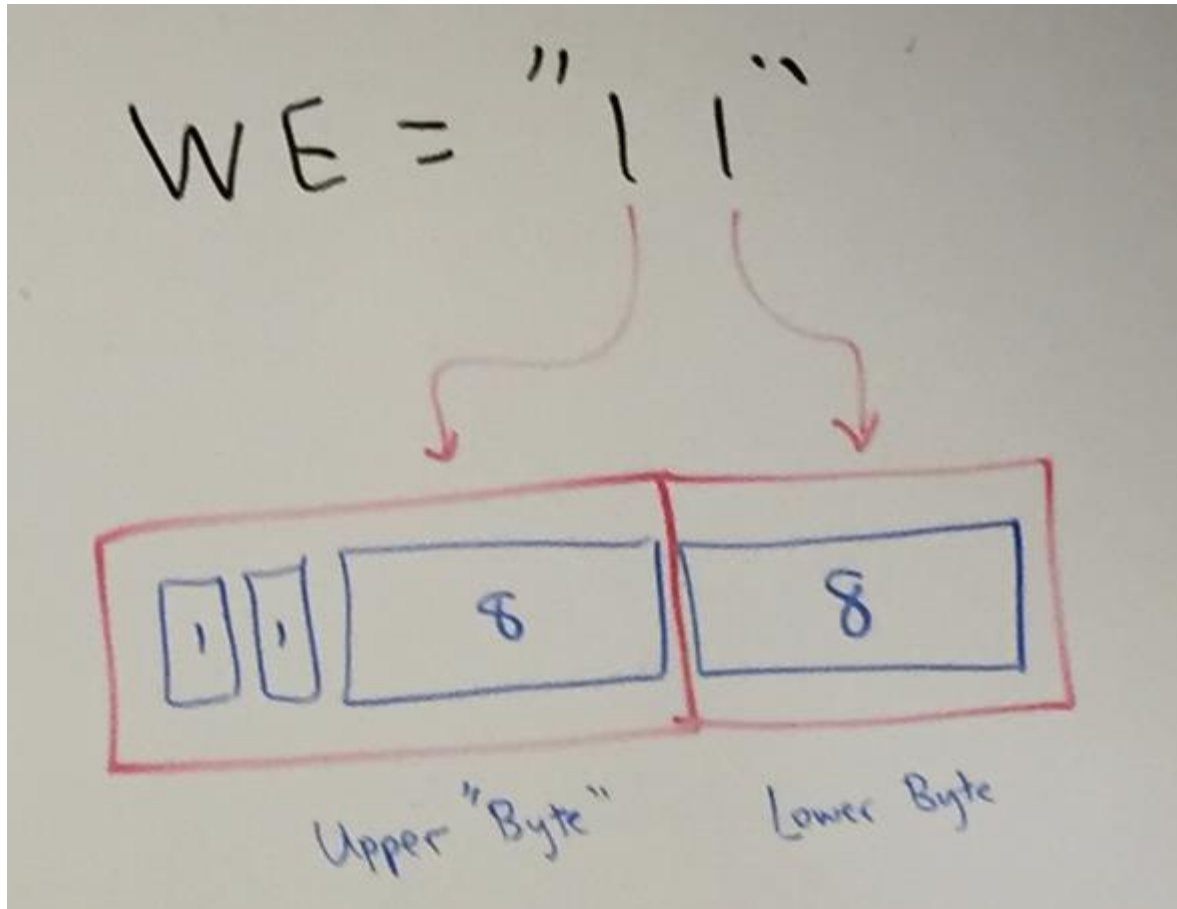



Datapath and Control – BRAM Example Instantiation

-- Reference: Vivado Design Suite 7 Series FPGA Libraries Guide
-- UG953 (v 2012.4) July 25, 2012
--
-- Page: 10

```
sampleMemory: BRAM_SDP_MACRO
  generic map (
    BRAM_SIZE => "18Kb",           -- Target BRAM, "18Kb" or "36Kb"
    DEVICE => "7SERIES",          -- Target device: "VIRTEX5", "VIRTEX6", "SPARTAN6, 7SERIES"
    DO_REG => 0,                  -- Optional output register disabled
    INIT => X"000000000000000000", -- Initial values on output port
    INIT_FILE => "NONE",          -- Not sure how to initialize the RAM from a file
    WRITE_WIDTH => 18,            -- Valid values are 1-72 (37-72 only valid when BRAM_SIZE="36Kb")
    READ_WIDTH => 18,            -- Valid values are 1-72 (37-72 only valid when BRAM_SIZE="36Kb")
    SIM_COLLISION_CHECK => "NONE", -- Collision check enable "ALL", "WARNING_ONLY",
                                   "GENERATE_X_ONLY" or "NONE"
    SRVAL => X"000000000000000000") -- Set/Reset value for port output
```



Datapath and Control – BRAM

Instantiation continued

port map (

```
DO => readOutput,  
RDADDR => vecAddrRead,  
RDCLK => clk,  
RST => reset,  
RDEN => cw(5),  
REGCE => '1',  
DI => writeInput,  
WE => cw(3 downto 2),  
WRADDR => vecAddrWrite,  
WRCLK => clk,  
WREN => cw(4));
```

```
-- Output read data port, width defined by READ_WIDTH parameter  
-- Input address, width defined by port depth  
-- 1-bit input clock  
-- active high reset  
-- read enable  
-- 1-bit input read output register enable - ignored  
-- Input data port, width defined by WRITE_WIDTH parameter  
-- since RAM is byte read, this determines high or low byte  
-- Input write address, width defined by write port depth  
-- 1-bit input write clock  
-- 1-bit input write port enable
```



```
process (clk)
begin
    if (rising_edge (clk)) then
        if (n_reset = '0') then
            addrWrite <= (others => '0');
        elsif (cw(1 downto 0) = "01") then
            addrWrite <= addrWrite + 1;
        elsif (cw(1 downto 0) = "11") then
            addrWrite <= (others => '0');
        end if;
    end if;
end process;

addrRead <= addrWrite - 1; -- Have the read follow the writes
writeInput <= "10101010101010" & vecAddrWrite(3 downto 0); -- Provide some changing data input

reset <= not n_reset; * -- BRAM reset is active high
vecAddrWrite <= std_logic_vector(addrWrite); -- type conversion (address are std_logic_vector)
vecAddrRead <= std_logic_vector(addrRead);
```



Datapath and Control – Class Activity

■ Class Activity:

- Determine what will happen inside the RAM defined above when subject to the following signals.

-- vecAddrRead = vecAddrWrite - 1

-- writeInput <= "10101010101010" & vecAddrWrite(3 downto 0);

cw(5) <= '1', '0' after 7 us, '1' after 8 us; -- READ ENABLE


cw(4) <= '1', '0' after 3 us, '1' after 4 us; -- WRITE ENABLE

cw(3 downto 2) <= "11", "10" after 4 us, "01" after 5 us, "11" after 6 us; -- BYTE WRITE ENABLE


cw(1 downto 0) <= "01"; -- COUNTER CONTROL



Datapath and Control - BRAM

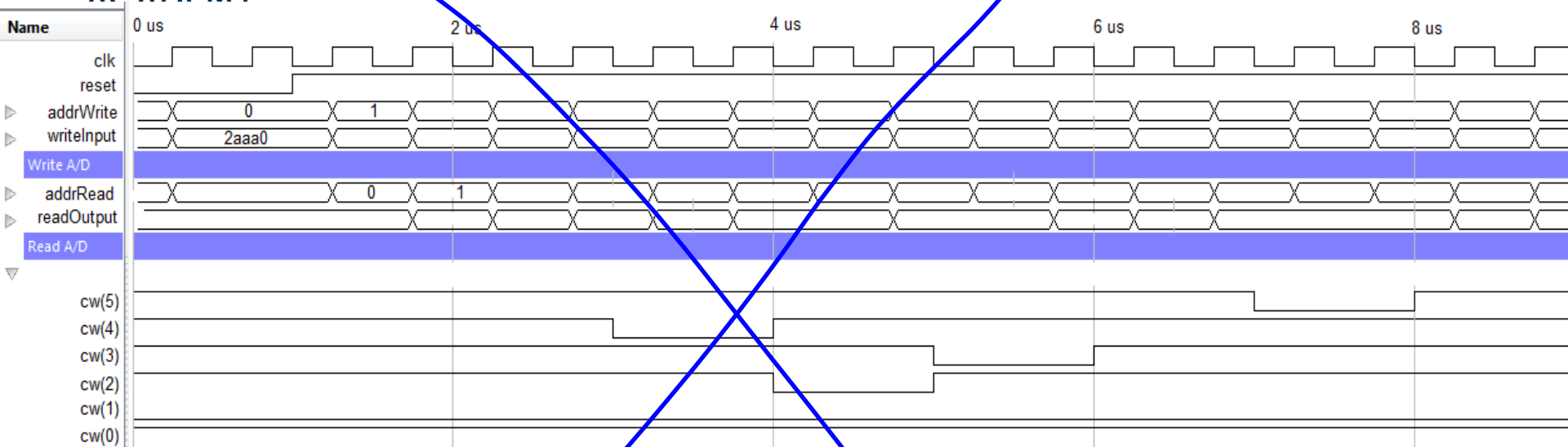

| Addr | writeInput | WREN=cw (4) | WE=cw (3, 2) | RDEN=cw (5) | readOutput |
|------|------------|-------------|--------------|-------------|------------|
| 0x0 | 0x2AAA0 | | | | |
| 0x1 | 0x2AAA1 | | | | |
| 0x2 | | | | | |
| 0x3 | | | | | |
| 0x4 | | | | | |
| 0x5 | | | | | |
| 0x6 | | | | | |
| 0x7 | | | | | |
| 0x8 | 0x2AAA8 | | | | |
| 0x9 | | | | | |
| 0xA | | | | | |
| 0xB | | | | | |
| 0xC | | | | | |
| 0xD | | | | | |
| 0xE | 0x2AAAE | | | | |
| 0xF | | | | | |

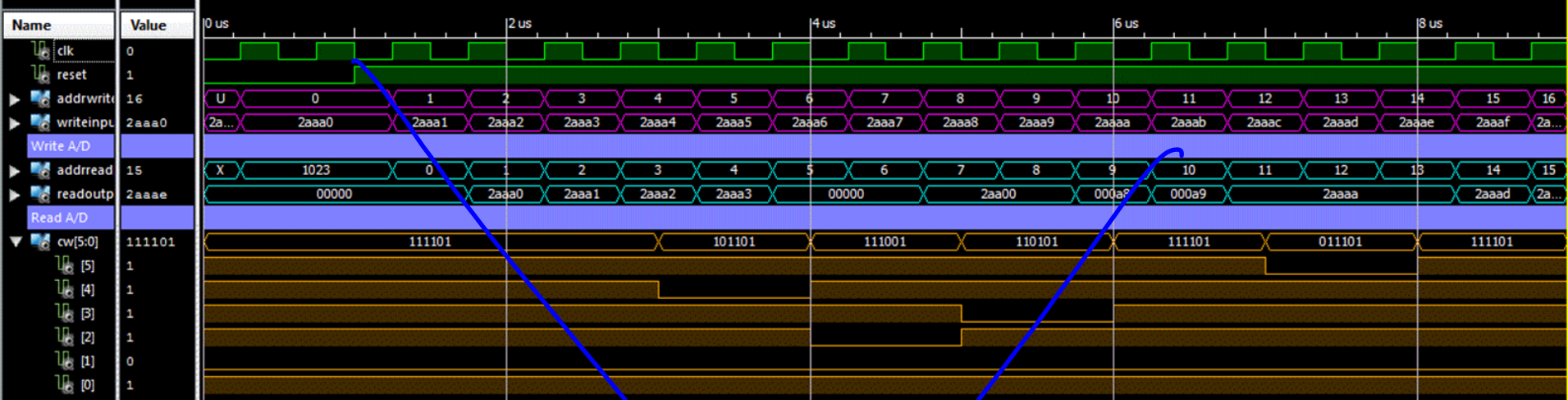

| Addr | Write Input | WREN=cw(4) | WE=cw(3,2) | RDEN=cw(5) | Read Value |
|------|-------------|------------|------------|------------|------------|
| 0x0 | 0x2AAA0 | 1 | 11 | 1 | 0x2AAA0 |
| 0x1 | 0x2AAA1 | 1 | 11 | 1 | 0x2AAA1 |
| 0x2 | 0x2AAA2 | 1 | 11 | 1 | 0x2AAA2 |
| 0x3 | 0x2AAA3 | 1 | 11 | 1 | 0x2AAA3 |
| 0x4 | 0x2AAA4 | 0 | 11 | 1 | 0x00000 |
| 0x5 | 0x2AAA5 | 0 | 11 | 1 | 0x00000 |
| 0x6 | 0x2AAA6 | 1 | 10 | 1 | 0x2AA00 |
| 0x7 | 0x2AAA7 | 1 | 10 | 1 | 0x2AA00 |
| 0x8 | 0x2AAA8 | 1 | 01 | 1 | 0x000A8 |
| 0x9 | 0x2AAA9 | 1 | 01 | 1 | 0x000A9 |
| 0xA | 0x2AAAA | 1 | 11 | 1 | 0x2AAAA |
| 0xB | 0x2AAAB | 1 | 11 | 0 | 0x2AAAA |
| 0xC | 0x2AAAC | 1 | 11 | 0 | 0x2AAAA |
| 0xD | 0x2AAAD | 1 | 11 | 1 | 0x2AAAD |
| 0xE | 0x2AAAE | 1 | 11 | 1 | 0x2AAAE |
| 0xF | 0x2AAAF | 1 | 11 | 1 | 0x2AAAF |



Datapath and Control - Packages

- Packages are a nice way to hide lots of component declarations
- Redundancy is one of the main contributors of complexity in software is redundancy.
- Having an entities declaration in several different architectures is redundant.
- Pulling all these declarations into one file eliminates this redundancy and make the code much easier to maintain and update.
- So how do you create a Package?



Datapath and Control - Packages

- Packages – Package for Lab 2
 - http://ece.ninja/383/lecture/code/lab2_pack.vhdl
- Include this at the top of your file:
use work.lab2Parts.all; -- all my components are declared here

2-Line Handshake

- In most cases, digital systems require data from the external world in order to perform their tasks.
- In cases where the digital system and the outside world operate on independent clocks, the transfer of data is complicated by the lack of a common clock.
- To understand how a reliable transfer of data can be performed in this circumstance, consider the following scenario of a producer trying to deliver a packet of candies to a consumer.

Figure 12.2: A timing diagram of a data transfer between a producer and a consumer.



2-Line Handshake

 


Figure 12.2: A timing diagram of a data transfer between a producer and a consumer.



2-Line Handshake

- This protocol, regardless of who is the producer or consumer, is called a two-line handshake because the communicating agents must have two, coordinating signals Request (REQ) and Acknowledge (ACK) and at least one data line.
- REQ signal - used by the active agent to signal a readiness to perform a data transfer.
- ACK signal - used by the passive agent to acknowledge the data has been transferred.


Figure 12.2: A timing diagram of a data transfer between a producer and a consumer.

2-Line Handshake

- An algorithm description of the two-line handshake for a digital circuit which is the passive consumer is shown below.
 1. while(REQ==0); // Do nothing but wait
 2. register = DATA // Latch the data
 3. ACK=1; // Acknowledge the producer
 4. while(REQ==1); // Do nothing but wait
 5. ACK=0; // Acknowledge the producer
- In Line 1 and Line 4, the body of the while loops are empty; there is nothing to do but wait.
- Furthermore, with respect to the external world, the ACK and REQ signals act as status and command bits, respectively.
- The algorithm above is translated into datapath and control in Figure 12.3.

Figure 12.2: A timing diagram of a data transfer between a producer and a consumer.

2-Line Handshake

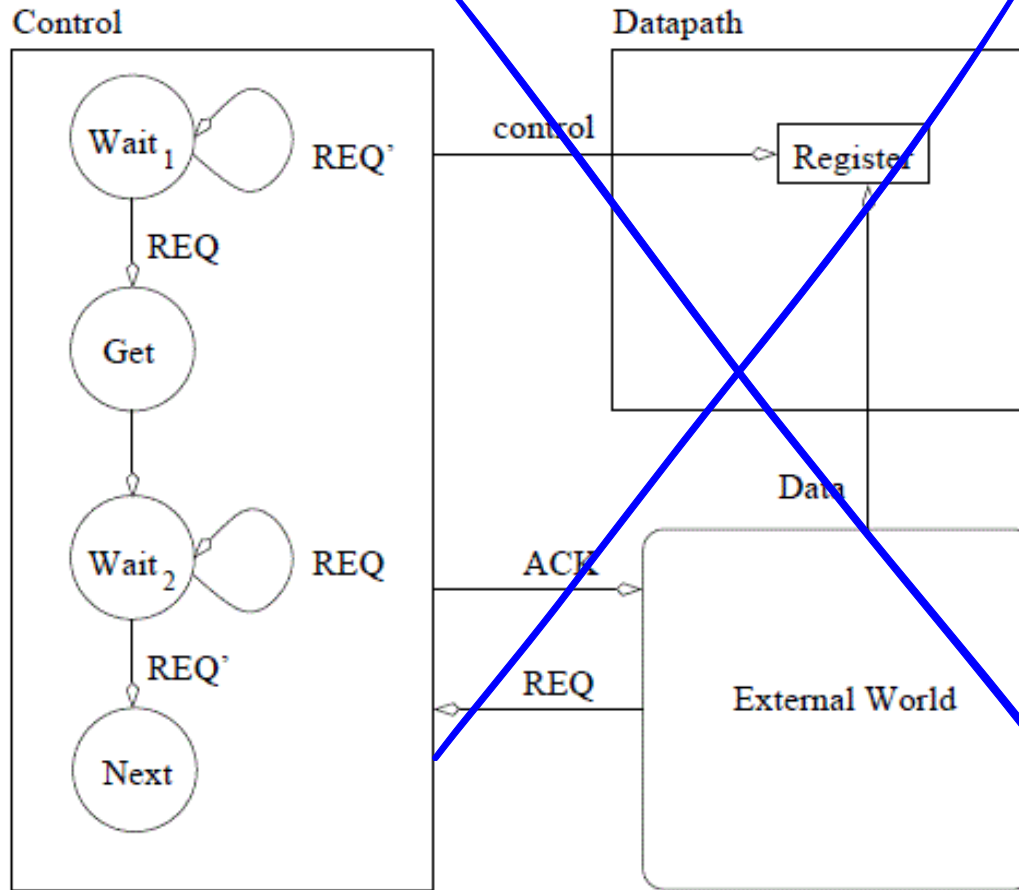

1. `while(REQ==0);`
// Do nothing but wait
2. `register = DATA`
// Latch the data
3. `ACK=1;`
// Acknowledge the producer
4. `while(REQ==1);`
// Do nothing but wait
5. `ACK=0;`
// Acknowledge the producer

Figure 12.3: The datapath and control components required to implement a two-line handshake where the digital system is the passive consumer.



OLD

Datapath and Control – Exercise—HW#8b

- Build a circuit to read in an 8-bit KEY using a two-line handshake; the circuit is a passive consumer.
- The circuit should search an 18kx16 RAM, counting the number of words that match KEY.
- Assume the RAM is preloaded with data and it can respond to a read request with valid data within one clock

```
1. while(1) {  
2.   while(REQ == 0);  
3.   KEY = data;  
4.   ACK = 1;  
5.   while(REQ == 1);  
6.   ACK = 0;  
7.   match = 0;  
8.   for(i=0; i<1024; i++) {  
9.     MBR = RAM[i];  
10.    if (MBR == KEY) {  
11.      match=match+1;  
12.    } // end if  
13.  } // end for  
14. } // end while
```

HW8b2

For 1023 memory locations in a BRAM, build a circuit to read in a 16-bit DATA_IN whenever READY goes HIGH, increment the data by 7, store the value in the current memory location, and then read the data stored at this memory location back out and store it in an output register called DATA_OUT. Then repeat for the next memory location.

You are given hw8b2_[tb.vhdl](#),


You are given partial files for HW8b2_design_template.pptx, hw8b2_[cu.vhdl](#), and hw8b2_dp.vhdl

Which you will need to complete.

Here is the mini-C to implement:

```
1.  for(i=0; i<1023; i++) {      // for every memory location
2.      while(READY==0);        // wait for ready (rising edge)
4.      RAM[i] = DATA_IN + 7; // store data + 7 in memory location i
5.      DATA_OUT = RAM[i];     // read data from memory location i
6.      while(READY==1);        // wait for ready (falling edge)
7. } // end for
```


Example Simulation Plot

 




- **For next class**
 - **Do HW8b**
 - **Prep for lab2**
 - **Read the assignment**
 - **Copy your lab1 files and given lab2 files, and build a lab2 project in vivado**
 - **GateCheck 1 due EOC next lesson**
- **Rest of Class today?**
 - **Work on HW8b?**
 - **Intro to Lab#2**
 - **GR Review?**
 - **HW8?**




Homework #8

| Name | Value |
|----------------|-------------|
| clk | 0 |
| reset | 1 |
| kbclk | 1 |
| kbdata | 1 |
| state | waitstart |
| sw | 0 |
| busy | 0 |
| shiftreg[10:0] | 11000101100 |
| scan[7:0] | 16 |
| keycntr[5:0] | 0 |

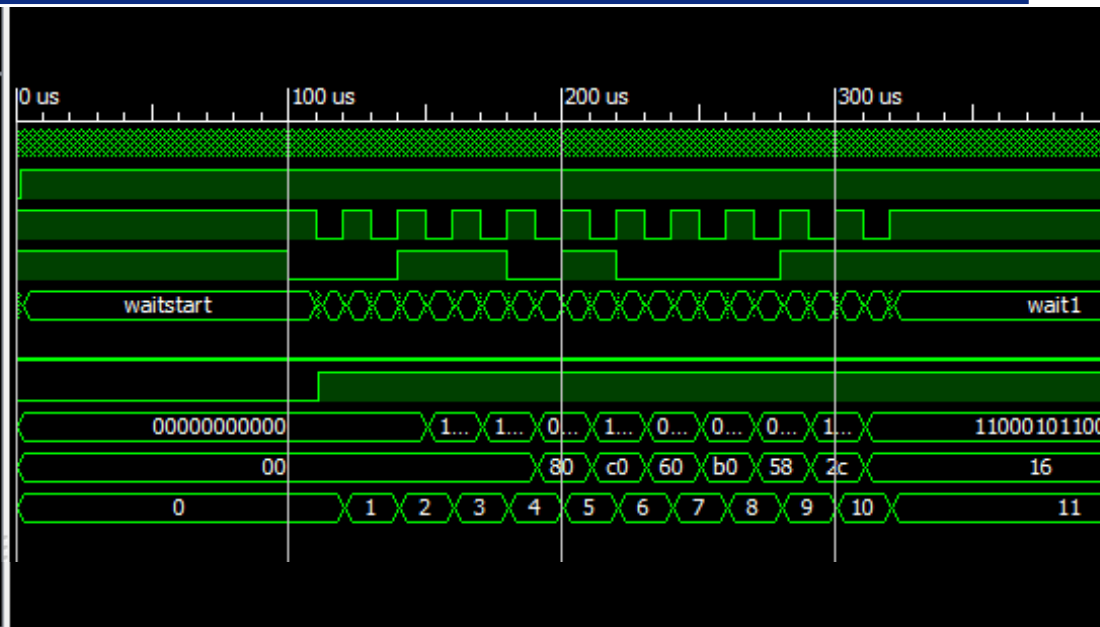

| Name | Value |
|----------------|-------------|
| clk | 0 |
| reset | 1 |
| kbclk | 1 |
| kbdata | 1 |
| state | waitstart |
| sw | 0 |
| busy | 0 |
| shiftreg[10:0] | 11000101100 |
| scan[7:0] | 16 |
| keycntr[5:0] | 0 |

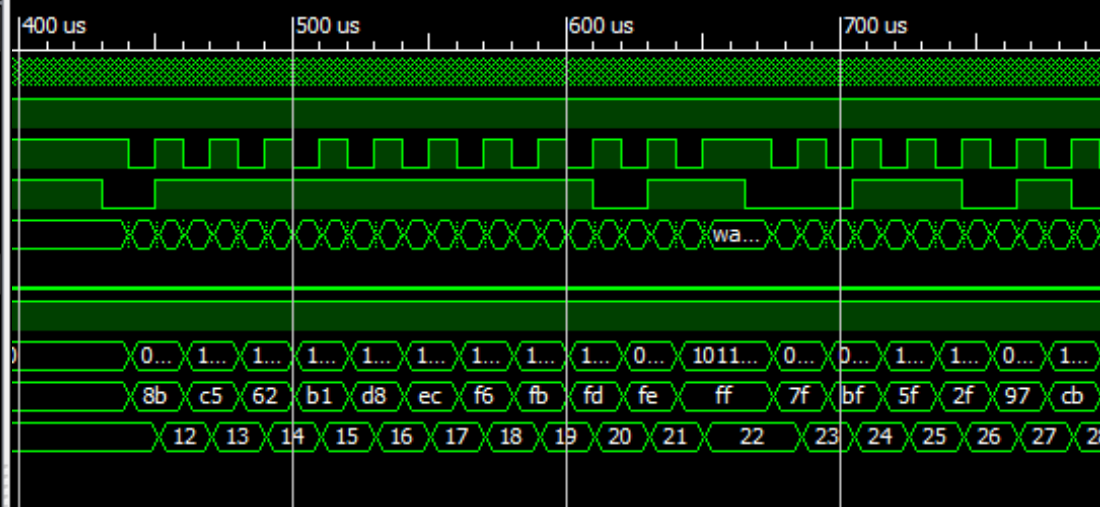



UNITED STATES
AIR FORCE
ACADEMY

HW8 solution?